


CSE 241

Lecture 3

 **University at Buffalo**
School of Engineering and Applied Sciences


Overview for this lecture

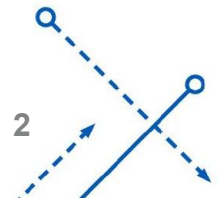- Reminders
- Finish SOP/POS Problem
- Karnaugh Map
- More Logic Gates




Reminders

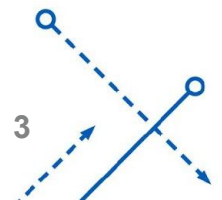- HW1 Due at 11:59pm tonight
 - Closes out tomorrow at 11:59pm
- First Recitation Today
- Next Monday is Exam Prep
- Next Wednesday is the Exam



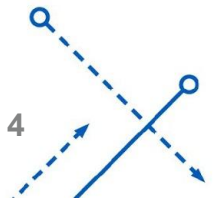
Exercise

$F(A,B,C) = \Pi(0,2,3,5)$; find canonical SOP and POS forms equations and gate diagrams. Use only 2 input logic gates.




Reminder

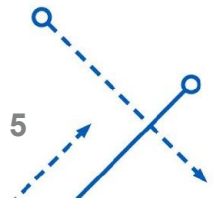- Any logic function can be designed from a truth table in either of two canonical forms: SOP and POS.
- For SOP
 - Find minterms for rows with $f = 1$.
 - Make one AND for each minterm.
 - OR the ANDs together.
- For POS
 - Find maxterms for rows with $f = 0$.
 - Make one OR for each maxterm.
 - AND the ORs together.



Karnaugh Map (K-Map)

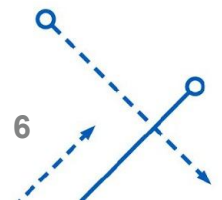- Visual mapping tool
- Combines adjacent 1's (for SOP) into pairs
 - vertically
 - horizontally
 - NOT diagonally
- Combines adjacent pairs into blocks of 4, 8, etc.
- For POS, we combine 0's




Two Variable Minterms

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

(a) Truth table

		x_1	
		0	1
x_2	0	m_0	m_2
	1	m_1	m_3

(b) Karnaugh map

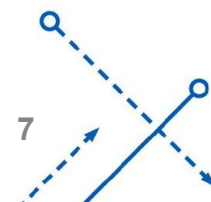


Three Variable Minterms

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table


		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

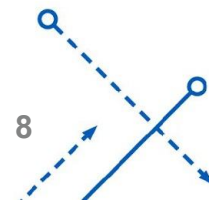


Labeling 1's on SOP K-Maps

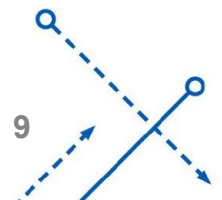
- 1s on SOP K-maps are minterms
- they are labeled the way minterms are
 - if row or column heading for a variable X is
 - $0 \Rightarrow X'$
 - $1 \Rightarrow X$



Three Variable K-Maps

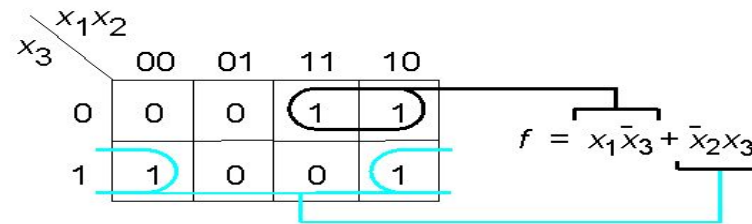


(a) The function of Figure 2.18

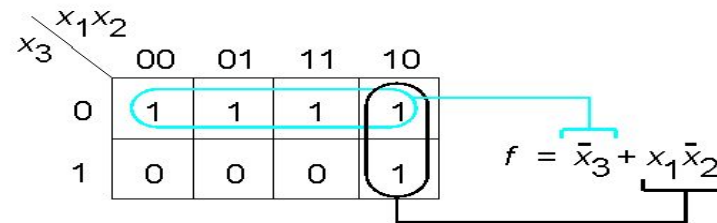

(b) The function of Figure 4.1


Let's Practice Some K-Map Drawing

$$F(A, B, C) = \sum(1, 2, 7)$$

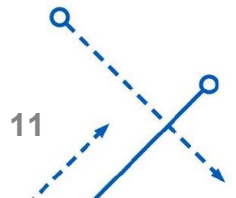


Exercise

$$F(A, B, C) = \sum(0, 1, 6, 7)$$

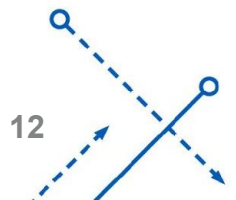


Terms

- literal - true or complemented variable, e.g. A , C'
- implicant - product that if 1 means function is 1
 - can be minterm, pair, etc., e.g. AB' , C , $AC'D$
- prime implicant (PI) - implicant that can't be combined with another implicant;
 - \Rightarrow fewest literals for given 1
 - \Rightarrow largest block for given 1
- essential prime implicant (EPI) - PI needed for f
- distinguished 1 - 1 included in just one PI
- cover - group of implicants that include all 1s of f

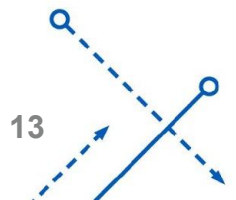

Terminology Example

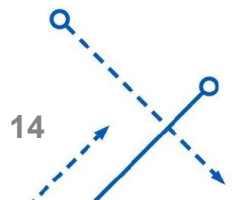- $F(A,B,C) = \Sigma(0,1,4,6)$
- All Prime Implicants:
 - $A'B', AC', B'C'$
- Distinguished 1s:
 - 1, 6
- Essential PI:
 - $A'B', AC'$



Terminology Exercise

- Find distinguished 1s, PI and EPI for

$$f(A,B,C) = \Sigma(2,4,5,6)$$

- PI
- distinguished 1s
- EPI



Four Variable Minterms

$x_3 x_4$ \ $x_1 x_2$		x_1			
		00	01	11	10
x_3	00	m_0	m_4	m_{12}	m_8
	01	m_1	m_5	m_{13}	m_9
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	m_{14}	m_{10}
		x_2			
		x_4			

4 Variable K-Map

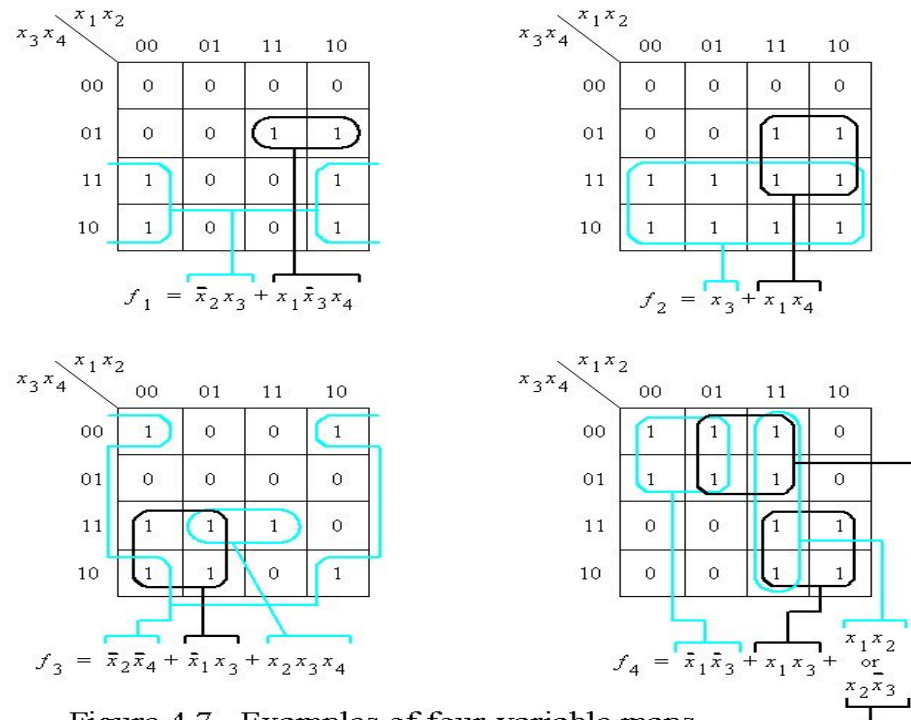


Figure 4.7. Examples of four-variable maps.

Let's Practice A Few

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 7, 13, 15)$$



Exercise


$$F(A, B, C, D) = \sum(1, 2, 7, 9, 10, 11, 15)$$

5 Variable K-Map

- $f(A,B,C,D,E)$
- Use two 4-variable K-maps for B,C,D,E
 - one for $A = 0$
 - one for $A = 1$
- Map for $A = 1$ has cell numbers 16 higher correspondingly.
- Combine adjacent 1s in 3 dimensions
 - vertically
 - horizontally
 - out of the page



5 Variable K-Map

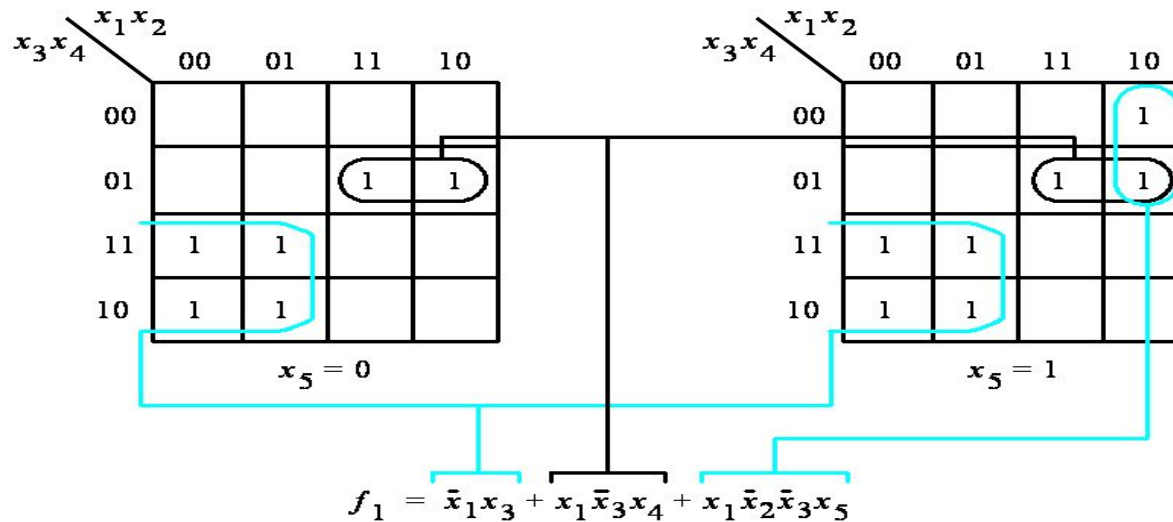

Let's Practice One

$$F(A, B, C, D, E) = \sum(1, 2, 7, 12, 16, 18, 22, 23, 26, 29, 31)$$



Six Variable K-Map

- $f(A,B,C,D,E,F)$
 - Use four 4-variable K-maps for C,D,E,F
 - one for A,B = 0,0
 - one for A,B = 0,1
 - one for A,B = 1,0
 - one for A,B = 1,1
 - Maps have corresponding cell numbers from 0,16,32,48
 - Combine adjacent 1s in 3 dimensions
 - vertically
 - horizontally
 - out of the page
- This is evil, we won't go beyond 5 variables



Higher Variable K-Maps

- 5- and 6-variable K-maps are borderline for identifying patterns.
- Meaning we'll only make you do it a little.
- And no 6-variable maps.
- Beyond 6 variables K-maps are not useful.
- Tabular techniques are preferred.



Minimization Procedure

- Map the function f .
- Find all PI, largest blocks first.
- Find distinguished 1s and EPI.
- Start implementing f with EPI.
- Do EPI include all 1s of f ?
- If yes, f is done.
- If no, select a minimum number of other PI.



Minimization Guidelines

- Always prefer larger blocks to smaller.
- In 4-variable f , block of 4 has two literals, pair has three.
 - When EPI do not cover f , use best judgment.
 - If in doubt, arbitrarily add another PI and then select from remaining.
- To be sure of minimum cost, try again with each other nonessential PI.



Functions with no EPI

- Can be cyclic
- Arbitrarily start with one PI and then get others as necessary.
- Then try starting with each other PI until you find minimal circuit.
- In other words, “guess and check”.



Let's Do A Bit More Practice

$$F(A, B, C, D) = \sum(1, 2, 9, 13, 14)$$

Let's also note:

- PI
- distinguished 1s
- EPI




What About POS?

- 0s on POS K-maps are maxterms
 - Therefore, they are labeled the way maxterms are
- if row or column heading for a variable X is
 - $0 \Rightarrow X$
 - $1 \Rightarrow X'$




POS Minimization

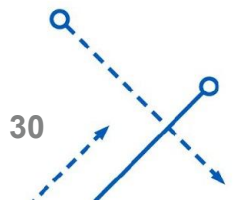- Just like SOP except works with 0s of f .
- Terms are same except implicates and distinguished 0s.
- Use sum term labeling. ($0 \Rightarrow x$, $1 \Rightarrow x'$)
- Map 0s of f .
- Find PI, largest blocks first.
- Find EPI and distinguished 0s.
- Implement f with EPI, adding other PI as necessary for minimal cost.



POS Example

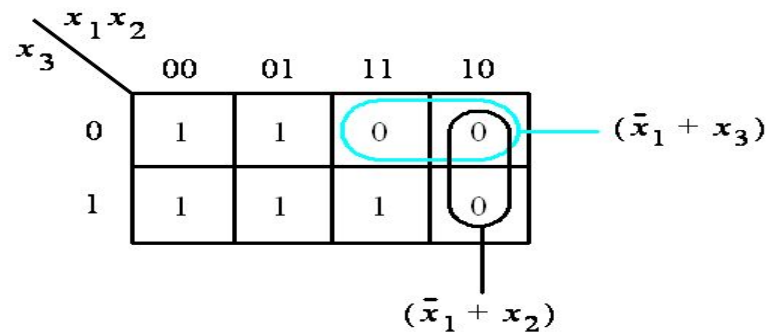

Another POS Example

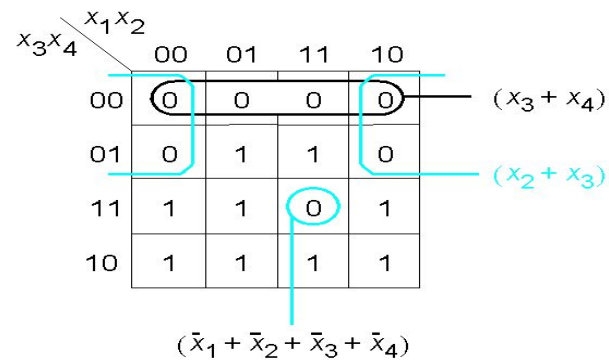


Figure 4.14. POS minimization of $f = \Pi M(0, 1, 4, 8, 9, 12, 15)$.


Let's Do A Little POS Practice - Example

$$F(x,y,z)=\prod(0,1,4,6)$$



Exercise

$$F(w,x,y,z)=\prod(0,2,7,8,12,15)$$

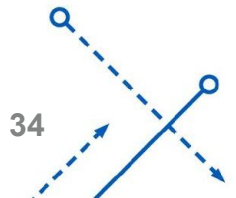

Incompletely Specified Functions

- don't care condition (d)--input condition that either
 - can't occur
 - or doesn't matter if it occurs.
- incompletely specified circuit
 - circuit with one or more don't cares
- Treat don't cares as 1s (for SOP) in forming PI
 - allows forming bigger blocks
- Ignore don't cares in selecting PI.
- Never select a PI only to cover a don't care!!



Example

- $F(A,B,C,D,E) = \Sigma(1,9,10,17,21,27) +$
 $d(3,5,11,25,26)$



Exercise


- $F(A,B,C,D) = \Sigma(1,6,7) +$
 $d(3,5,13,15)$

Let's Review Gate Diagrams Using K-Maps To Get the Minimized Form


$$F(A,B,C, D)=\sum(0,1,4,6,8,10,12,14,15)$$



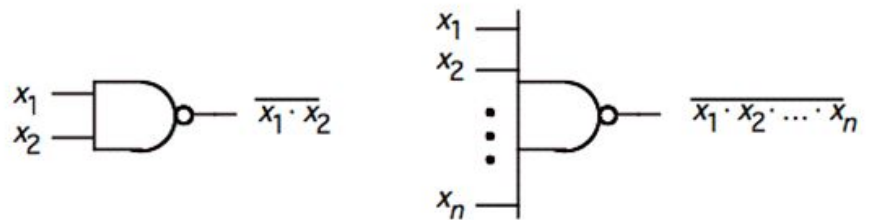Let's Expand Out Our Logic Gate Collection



(a) NAND gates

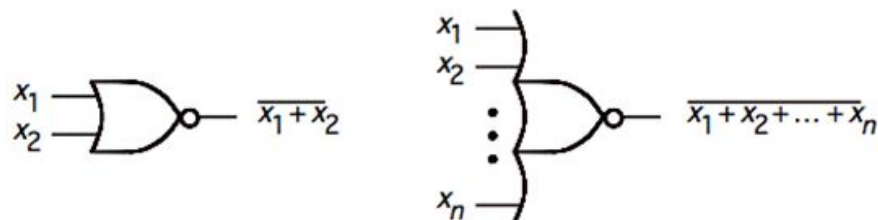



(b) NOR gates

Figure 2.20. NAND and NOR gates.




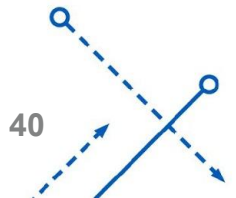- You can create any combinational function in two levels of logic using AND and OR and NOT.
- You can do all of the same functions using only NAND or NOR gates.




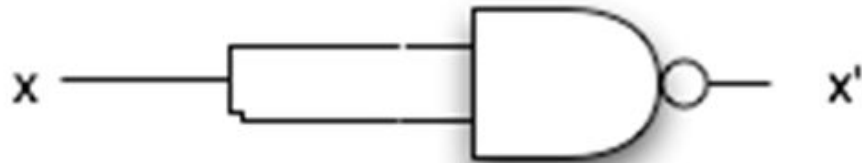

Replacing a NOT with NAND

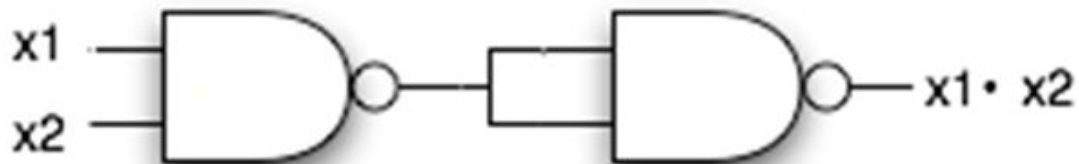


Replacing an AND with NAND

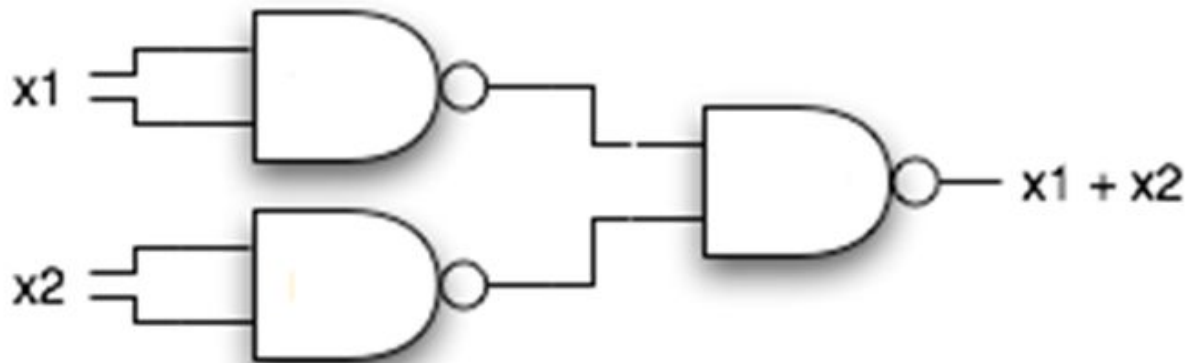


Replacing an OR with NAND



Replacing a NOT with NOR

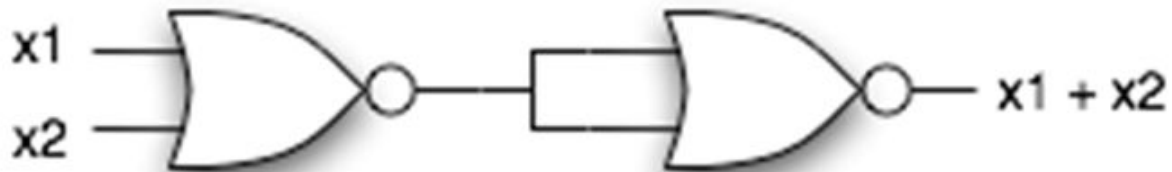


Replacing an OR with NOR

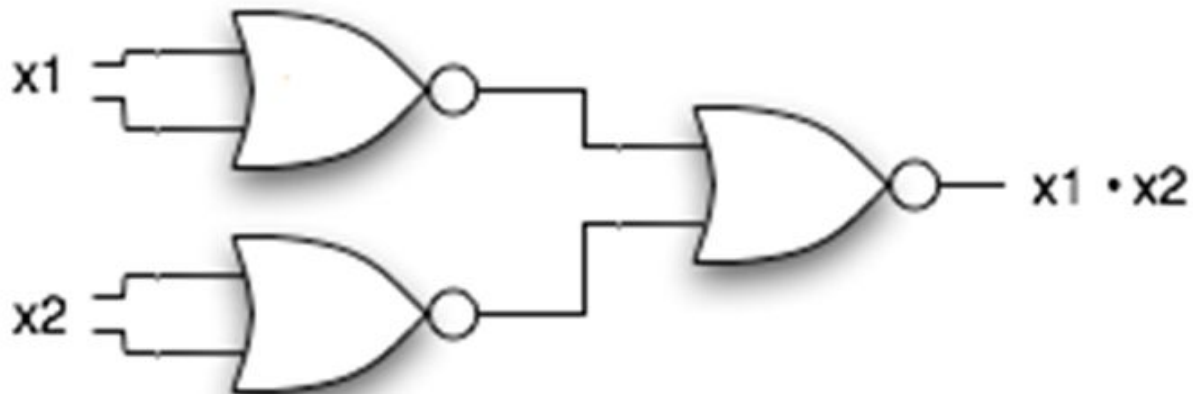

Replacing an AND with NOR

Reduction on Logic Diagrams

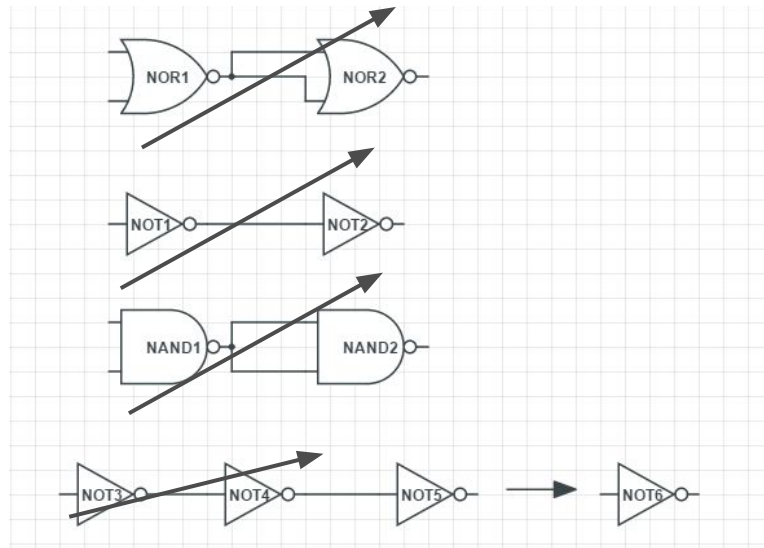




Let's Take That Last Example And...

Implement it with only 2 Input NAND Gates

Implement it with only 2 Input NOR Gates

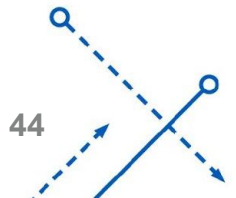


Exercise

Use K-Map to reduce and implement with only

- 2 input NAND Gates
- 2 input NOR Gates

$$F(X, Y, Z) = \sum(1, 2, 3, 7)$$

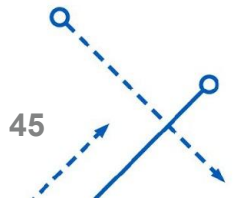

What Is Next

- Your Exam- This is the end of material for the exam
 - Monday
 - First half of class we will do new stuff
 - Second half of class we will do practice exam
 - This is done in small groups
 - Open resource
 - For credit
- Then What?
 - Putting this to use- Combinational Logic Circuits